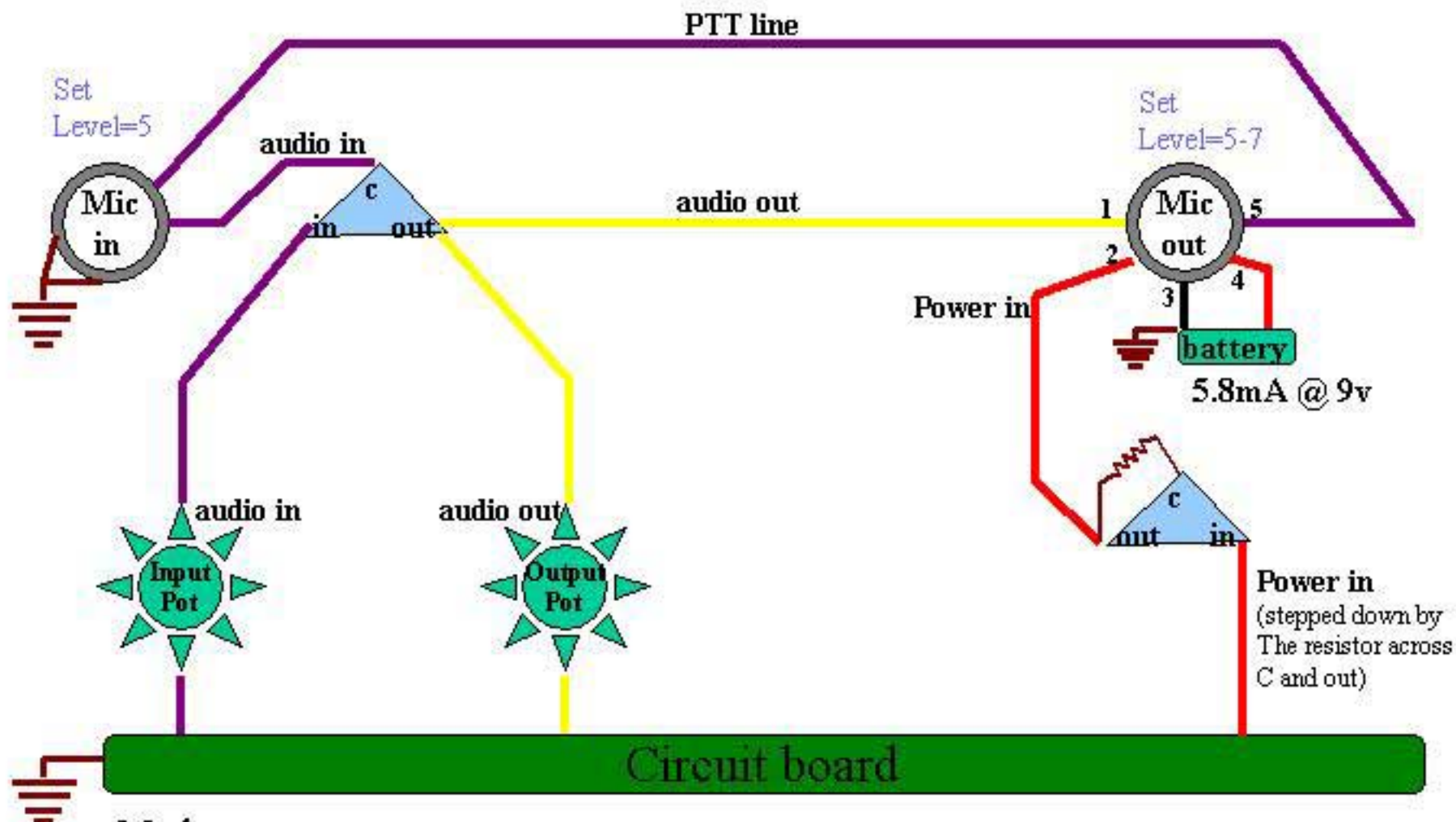


Datong RF Clipper c.1975 – simplified circuit



Mods:

- 4 pin mic skt replaced by 8 pin.
- External power skt provided with step down from 12v to 9v but this introduced RF feedback into the clipper and is unusable
- 82pF caps on mic skt between mic-chassis & ptt-chassis replaced with 100pF