

# 1

---

## *Introduction*

Wine is bottled poetry.

—Robert Louis Stevenson

Wine gives courage and makes men more apt for passion.

—Ovid

I made wine out of raisins so I wouldn't have to wait for it to age.

—Steven Wright

In this chapter we use a simple example to give an informal introduction to many of the concepts and design methods that are covered in this book. Each of the topics in this chapter is addressed more formally in much more detail in subsequent chapters.

### **1.1 PROBLEM SPECIFICATION**

In a small town in southern Utah, there's a little winery with a wine shop nearby. Being a small town in a county that thinks Prohibition still exists, there is only one wine patron. The wine shop has a single small shelf capable of holding only a single bottle of wine. Each hour, on the hour, the shopkeeper receives a freshly made bottle of wine from the winery which he places on the shelf. At half past each hour, the patron arrives to purchase the wine, making space for the next bottle of wine. Now, the patron has learned that it is very important to be right on time. When he has arrived early, he has found

an empty shelf, making him quite irate. When he has arrived late, he has found that the shopkeeper drank the last bottle of wine to make room for the new bottle. The most frustrating experience was when he arrived at just the same time that the shopkeeper was placing the bottle on the shelf. In his excitement, he and the shopkeeper collided, sending the wine bottle to the floor, shattering it, so that no one got to partake of that lovely bottle of wine.

This synchronous method of wine shopping went on for some time, with all parties being quite happy. Then one day (in the mid-1980s), telephone service arrived in this town. This was a glorious invention which got the town really excited. The patron got a wonderful idea. He knew the winery could operate faster if only he had a way to purchase the wine faster. Therefore, he suggested to the shopkeeper, "Say, why don't you give me a call when the wine arrives?" This way he could avoid showing up too early, frustrating his fragile temperament. Shortly after the next hour, he received a call to pick up the wine. He was so excited that he ran over to the store. On his way out, he suggested to the shopkeeper, "Say, why don't you give the folks at the winery a call to tell them you have room for another bottle of wine?" This is exactly what the shopkeeper did; and wouldn't you know it, the wine patron got another call just 10 minutes later that a new bottle had arrived. This continued throughout the hour. Sometimes it would take 10 minutes to get a call while other times it would take as long as 20 minutes. There was even one time he got a call just five minutes after leaving the shop (fortunately, he lived very close by). At the end of the hour, he realized that he had drunk 5 bottles of wine in just one hour!

At this point, he was feeling a bit woozy, so he decided to take a little snooze. An hour later, he woke up suddenly quite upset. He realized that the phone had been ringing off the hook. "Oh my gosh, I forgot about the wine!" He rushed over, expecting to find that the shopkeeper had drunk several bottles of his wine, but to his dismay, he saw one bottle on the shelf with no empties laying around. He asked the shopkeeper, "Why did they stop delivering wine?" The shopkeeper said, "Well, when I did not call, they decided that they had better hold up delivery until I had a place on my shelf."

From that day forward, this asynchronous method of wine shopping became the accepted means of doing business. The winery was happy, as they sold more wine (on average). The shopkeeper's wife was happy, as the shopkeeper never had to drink the excess. The patron was extremely happy, as he could now get wine faster, and whenever he felt a bit overcome by his drinking indiscretion, he could rest easy knowing that he would not miss a single bottle of wine.

## 1.2 COMMUNICATION CHANNELS

One day a VLSI engineer stopped by this small town's wine shop, and he got to talking with the shopkeeper about his little business. Business was



Fig. 1.1 Channels of communications.

good, but his wife kept bugging him to take that vacation to Maui he had been promising for years and years. He really did not know what to do, as he did not trust anyone to run his shop for him while he was away. Also, he was a little afraid that if he wasn't a little careful, the winery and patron might realize that they really did not need him and could deal with each other directly. He really could not afford that.

The VLSI engineer listened to him attentively, and when he was done announced, "I can solve all your problems. Let me design you a circuit!" At first, the shopkeeper was quite skeptical when he learned that this circuit would be powered by electricity (a new magical force that the locals had not completely accepted yet). The engineer announced, "It is really quite simple, actually." The engineer scribbled a little picture on his napkin (see Figure 1.1). This picture shows two *channels* of communication which must be kept synchronized. One is between the winery and the shop, and another is between the shop and the patron. When the winery receives a request from the shop over the *WineryShop communication channel*, the winery sends over a bottle of wine. This can be specified as follows:

```

Winery:process
begin
    send(WineryShop,bottle);
end process;
  
```

Note that the **process** statement implies that the *winery* loops forever sending bottles of wine. The wine patron, when requested by the shop over the *ShopPatron* communication channel, comes to receive a bottle of wine, which is specified as follows:

```

Patron:process
begin
    receive(ShopPatron,bag);
end process;
  
```

Now, what the shopkeeper does as the middleman (besides mark up the price) is provide a buffer for the wine to allow the winery to start preparing its next bottle of wine. This is specified as follows:

```

Shop:process
begin
    receive(WineryShop,shelf);
    send(ShopPatron,shelf);
end process;
  
```

These three things together form a *specification*. The first two processes describe the types of folks the shopkeeper deals with (i.e., his *environment*). The last process describes the behavior of the shop.

### 1.3 COMMUNICATION PROTOCOLS

After deriving a channel-level specification, it is then necessary to determine a *communication protocol* that implements the communication. For example, the shopkeeper calls the winery to “request” a new bottle of wine. After some time, the new bottle arrives, “acknowledging” the request. Once the bottle has been shelved safely, the shopkeeper can call the patron to “request” him to come purchase the wine. After some time, the patron arrives to purchase the wine, which “acknowledges” the request. This can be described as follows:

```
Shop:process
begin
    req_wine;    -- call winery
    ack_wine;    -- wine arrives
    req_patron;  -- call patron
    ack_patron;  -- patron buys wine
end process;
```

To build a VLSI circuit, it is necessary to assign signal wires to each of the four operations above. Two of the wires go to a device to place the appropriate phone call. These are called *outputs*. Another wire will come from a button that the wine delivery boy presses when he delivers the wine. Finally, the last wire comes from a button pressed by the patron. These two signals are *inputs*. Since this circuit is digital, these wires can only be in one of two states: either '0' (a low-voltage state) or '1' (a high-voltage state). Let us assume that the actions above are signaled by the corresponding wire changing to '1'. This can be described as follows:

```
Shop:process
begin
    assign(req_wine,'1');    -- call winery
    guard(ack_wine,'1');     -- wine arrives
    assign(req_patron,'1');  -- call patron
    guard(ack_patron,'1');   -- patron buys wine
end process;
```

The function `assign` used above sets a signal to a value. The function `guard` waits until a signal attains a given value. There is a problem with the specification given above in that when the second bottle of wine comes `req_wine` will already be '1'. Therefore, we need to reset these signals before looping back.

 


Fig. 1.2 (a) Waveform for a two-phase shop. (b) Waveform for a four-phase shop.

```

Shop_2Phase:process
begin
  assign(req_wine,'1');  -- call winery
  guard(ack_wine,'1');  -- wine arrives
  assign(req_patron,'1'); -- call patron
  guard(ack_patron,'1'); -- patron buys wine
  assign(req_wine,'0');  -- call winery
  guard(ack_wine,'0');  -- wine arrives
  assign(req_patron,'0'); -- call patron
  guard(ack_patron,'0'); -- patron buys wine
end process;

```

When *req\_wine* changes from '0' to '1', a phone call is placed, and when it changes again from '1' to '0', another call is placed. We call this *transition signaling*. It is also known as *two-phase* or *two-cycle signaling*, for obvious reasons. A waveform showing the behavior of a two-phase shop is shown in Figure 1.2(a). Another alternative is given below.

```

Shop_4Phase:process
begin
  assign(req_wine,'1');  -- call winery
  guard(ack_wine,'1');  -- wine arrives
  assign(req_wine,'0');  -- reset req_wine
  guard(ack_wine,'0');  -- ack_wine resets
  assign(req_patron,'1'); -- call patron
  guard(ack_patron,'1'); -- patron buys wine
  assign(req_patron,'0'); -- reset req_patron
  guard(ack_patron,'0'); -- ack_patron resets
end process;

```

This protocol is called *level signaling* because a call is placed when the request signal is '1'. It is also called *four-phase* or *four-cycle signaling*, since it takes four transitions to complete. A waveform showing the behavior of a

four-phase shop is shown in Figure 1.2(b). Although this protocol may appear to be a little more complex in that it requires twice as many transitions of signal wires, it often leads to simpler circuitry.

There are still more options. In the original protocol, the shop makes the calls to the winery and the patron. In other words, the shop is the *active* participant in both communications. The winery and the patron are the *passive* participants. They simply wait to be told when to act. Another alternative would be for the winery to be the active participant and call the shop when a bottle of wine is ready, as shown below.

```
Shop_PA:process
begin
  guard(req_wine,'1');    -- winery calls
  assign(ack_wine,'1');   -- wine is received
  guard(req_wine,'0');    -- req_wine resets
  assign(ack_wine,'0');   -- reset ack_wine
  assign(req_patron,'1'); -- call patron
  guard(ack_patron,'1');  -- patron buys wine
  assign(req_patron,'0'); -- reset req_patron
  guard(ack_patron,'0');  -- ack_patron resets
end process;
```

Similarly, the patron could be active as well and call when he has finished his last bottle of wine and requires another. Of course, in this case, the shopkeeper needs to install a second phone line.

```
Shop_PP:process
begin
  guard(req_wine,'1');    -- winery calls
  assign(ack_wine,'1');   -- wine is received
  guard(req_wine,'0');    -- req_wine resets
  assign(ack_wine,'0');   -- reset ack_wine
  guard(req_patron,'1');  -- patron calls
  assign(ack_patron,'1'); -- sells wine
  guard(req_patron,'0');  -- req_patron resets
  assign(ack_patron,'0'); -- reset ack_patron
end process;
```

Unfortunately, none of these specifications can be transformed into a circuit as is. Let's return to the initial four-phase protocol (i.e., the one labeled *Shop\_4Phase*). Initially, all the signal wires are set to '0' and the circuit is supposed to call the winery to request a bottle of wine. After the wine has arrived and the signal *req\_wine* and *ack\_wine* have been reset, the state of the signal wires is again all '0'. The problem is that in this case the circuit must call the patron. In other words, when all signal wires are set to '0', the circuit is in a state of confusion. Should the winery or the patron be called at this point? We need to determine some way to clarify this. Considering again the initial four-phase protocol, this can be accomplished by *reshuffling* the order in which these signal wires change. Although it is important that the wine

 


Fig. 1.3 Circuit for active/active shop.

arrives before the patron is called, exactly when the handshaking wires reset is less important. Rearranging the protocol as shown below allows the circuit always to be able to tell what to do. Also, the eager patron gets a call sooner. On top of that, it results in the very simple circuit shown in Figure 1.3.

```
Shop_AA_reshuffled:process
begin
  assign(req_wine,'1');    -- call winery
  guard(ack_wine,'1');     -- wine arrives
  assign(req_patron,'1');  -- call patron
  guard(ack_patron,'1');   -- patron buys wine
  assign(req_wine,'0');    -- reset req_wine
  guard(ack_wine,'0');     -- ack_wine resets
  assign(req_patron,'0');  -- reset req_patron
  guard(ack_patron,'0');   -- ack_patron resets
end process;
```

Alternatively, we could have reshuffled the protocol in which the shop passively waits for the winery to call but still actively calls the patron, as shown below. The resulting circuit is shown in Figure 1.4. The gate with a C in the middle is called a *Muller C-element*. When both of its inputs are '1', its output goes to '1'. Similarly, when both of its inputs are '0', its output goes to '0'. Otherwise, it retains its old value.

```
Shop_PA_reshuffled:process
begin
  guard(req_wine,'1');     -- winery calls
  assign(ack_wine,'1');    -- receives wine
  guard(ack_patron,'0');   -- ack_patron resets
  assign(req_patron,'1');  -- call patron
  guard(req_wine,'0');     -- req_wine resets
  assign(ack_wine,'0');    -- reset ack_wine
  guard(ack_patron,'1');   -- patron buys wine
  assign(req_patron,'0');  -- reset req_patron
end process;
```

Another curious thing about this protocol is that it waits for *ack\_patron* to be '0', but it is '0' to begin with. A guard in which its expression is already satisfied simply passes straight through. We call that first guard *vacuous* because it does nothing. However, the second time around, *ack\_patron* may actually have not reset at that point. Postponing this guard until this point

 


Fig. 1.4 Circuit for passive/active shop.

allows *ack\_patron* to be reset concurrently with *req\_wine* and *ack\_wine* being set. This increased concurrency can potentially improve the performance.

## 1.4 GRAPHICAL REPRESENTATIONS

Before describing how these circuits are derived, let us first consider an alternative way of looking at these specifications using graphs. The first method is to use an *asynchronous finite state machine* (AFSM). As an example, consider the active/active protocol from above (see *Shop\_AA\_reshuffled*): It can be represented as an AFSM, as shown in Figure 1.5(a), or in a tabular form called a *Huffman flow table*, shown in Figure 1.5(b). In the state machine, each node in the graph represents a state, and each arc represents a state transition. The state transition is labeled with the value of the inputs needed to make a state transition (these are the numbers to the left of the “/”). The numbers to the right of the “/” represent what the outputs do during the state transition. Starting in state 0, if both *ack\_wine* and *ack\_patron* are ‘0’, as is the case initially, the output *req\_wine* is set to ‘1’ and the machine moves into state 1. In state 1, the machine waits until *ack\_wine* goes to ‘1’, and then it sets *req\_patron* to ‘1’ and moves to state 2. The same behavior is illustrated in the Huffman flow table, in which the rows are the states and the columns are the input values (i.e., *ack\_wine* and *ack\_patron*). Each entry is labelled with the next state and next value of the outputs (i.e., *req\_wine* and *req\_patron*) for a given state and input combination. When the next state equals the current state, it is circled to indicate that it is stable.

Not all protocols can be described using an AFSM. The AFSM model assumes that inputs change followed by output and state changes in sequence. In the second design (see *Shop\_PA\_reshuffled*), however, inputs and outputs can change concurrently. For example, *req\_wine* may be set to ‘0’ while *req\_patron* is being set to ‘1’. Instead, we can use a different graphical method called



 


Fig. 1.5 (a) AFSM and (b) Huffman flow table for active/active shop (input/output vector is  $\langle ack\_wine, ack\_patron \rangle / \langle req\_wine, req\_patron \rangle$ ).

a *Petri net* (PN) to illustrate the behavior of the second design as shown in Figure 1.6(a).

In a Petri net, the nodes of the graph represent signal transitions. For example,  $req\_wine+$  indicates that  $req\_wine$  changes from '0' to '1'. Similarly,  $req\_wine-$  indicates that  $req\_wine$  changes from '1' to '0'. The arcs in this graph represent causal relationships between transitions. For example, the arc between  $req\_wine+$  and  $ack\_wine+$  indicates that  $req\_wine$  must be set to '1' before  $ack\_wine$  can be set to '1'. The little balls are called *tokens*, and a collection of tokens is called a *marking* of the Petri net. The initial marking is shown in Figure 1.6(a).

For a signal transition to occur, it must have tokens on all of its incoming arcs. Therefore, the only transition that may occur in the initial marking is  $req\_wine$  may be set to '1'. After  $req\_wine$  changes value, the tokens are removed from the incoming arcs and new tokens are placed on each outgoing arc. In this case, the token on the arc between  $ack\_wine-$  and  $req\_wine+$  would be removed, and a new token would be put on the arc between  $req\_wine+$  and  $ack\_wine+$ , as shown in Figure 1.6(b). In this marking,  $ack\_wine$  can now be set to '1', and no other signal transition is possible. After  $ack\_wine$  becomes '1', tokens are removed from its two incoming arcs and tokens are placed on its two outgoing arcs, as shown in Figure 1.6(c). In this new marking, there are two possible next signal transitions. Either  $req\_patron$  will be set to '1' or  $req\_wine$  will be set to '0'. These two signal transitions can occur in either order. The rest of the behavior of this circuit can be determined by similar analysis.

It takes quite a bit of practice to come up with a Petri-net model from any given word description. Another graphical model, called the *timed event/level* (TEL) *structure*, has a more direct correspondence with the word description. The TEL structure for the *Shop\_PAreshuffled* protocol is shown in Figure 1.7.

 


Fig. 1.6 PN for passive/active shop. (a) Initial marking, (b) after *req\_wine* goes to '1', and (c) after *ack\_wine* goes to '1'.

This TEL structure is composed of three processes that operate concurrently. There is one to describe the behavior of the winery, one to describe the behavior of the patron, and one to describe the behavior of the shop. The difference between a TEL structure and a Petri net is the ability to specify signal *levels* on the arcs. Each level expression corresponds to a **guard**, and each signal transition, or *event*, corresponds to an **assign** statement in the word description. There are four guards and four assign statements in the shop process, which correspond to four levels and four events in the graph for the shop. Note that the dashed arcs represent the initial marking and that in this initial marking all signals are '0'.

## 1.5 DELAY-INSENSITIVE CIRCUITS

Let's go back now and look at those circuits from before. How do we know they work correctly? Let's look again at our first circuit, redrawn in Figure 1.8

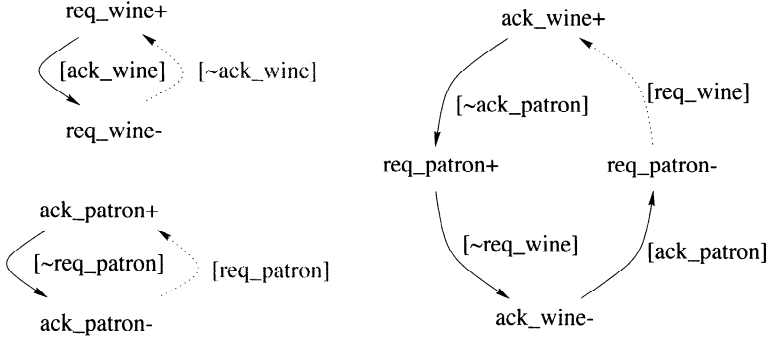


Fig. 1.7 TEL structure for passive/active shop.

 


Fig. 1.8 Complete circuit for active/active shop.

as a *complete circuit*, that is, with circuit elements for the environment. Let's also add *delay elements* (cigar-shaped boxes labeled "[0,inf]") to represent an unbounded delay. Now, recall that in the initial state all signal wires are set to '0'. In this state, the only thing that can happen is that *req\_wine* can be set to '1'. This is due to the '0' at the input of the inverter, which sets its output to '1'. We assume that this happens instantaneously. The delay element now randomly select a delay  $d$  between 0 and infinity. Let's say that it picks five minutes. The signal *req\_wine* now changes to '1' after five minutes has elapsed. At that point, the output of the attached buffer also changes to '1', but this change does not affect *ack\_wine* until a random delay later due to the attached delay element. If you play with this for awhile, you should be able to convince yourself that regardless of what delay values you choose, the circuit always behaves as you specified originally. We call such a circuit a *delay-insensitive circuit*. That is one whose correctness is independent of the delays of both the gates and the wires, even if these delays are unbounded. This mean that even during a strike of the grape mashers at the winery or when the patron is sleeping one off, the circuit still operates correctly. It is extremely robust.

Let's now look at the second circuit, redrawn with its environment in Figure 1.9. Again, in the initial state, the only transition which can occur is that

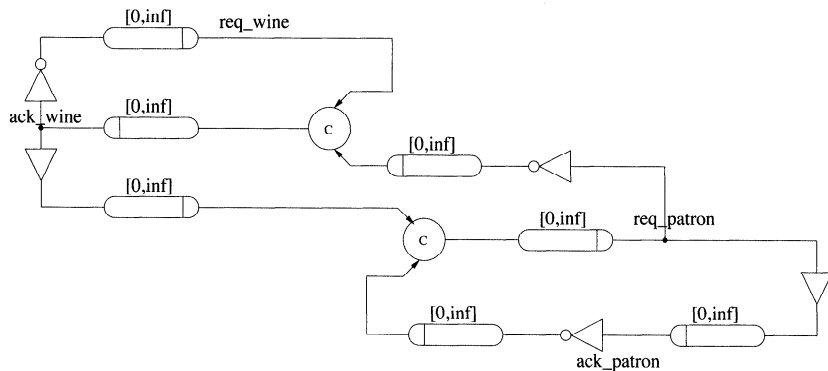


Fig. 1.9 Complete circuit for passive/active shop.

*req\_wine* can be set to '1' after some arbitrary delay. After *req\_wine* is '1', the next transition which can occur is that *ack\_wine* can be set to '1' after some delay. When *ack\_wine* is '1' though, there are two possible next transitions. Either *req\_wine* can go '0' or *req\_patron* can go to '1', depending on the choices made for the delay values in each delay element along the corresponding path. If you look at this circuit long enough, you can probably convince yourself that the circuit will behave as specified for whichever delay values are chosen each time around. This circuit is also delay-insensitive.

You may at this point begin to believe that you can always build a delay-insensitive circuit. Unfortunately, this is not the case. We are actually pretty fortunate with these two circuit designs. In general, if you use only single-output gates, this class of circuits is severely limited. In particular, you can only use buffers, inverters, and Muller C-elements to build delay-insensitive circuits. As an example, consider the circuit shown in Figure 1.10. It is a circuit implementation of a slightly modified version of our original four-phase protocol, where we have added a *state variable* to get rid of the state coding problem. The protocol is given below.

```

Shop_AA_state_variable:process
begin
  assign(req.wine,'1');    -- call winery
  guard(ack.wine,'1');     -- wine arrives
  assign(x,'1');          -- set state variable
  assign(req.wine,'0');    -- reset req.wine
  guard(ack.wine,'0');     -- ack.wine resets
  assign(req.patron,'1');  -- call patron
  guard(ack.patron,'1');   -- patron buys wine
  assign(x,'0');          -- reset state variable
  assign(req.patron,'0');  -- reset req.patron
  guard(ack.patron,'0');   -- ack.patron resets
end process;

```



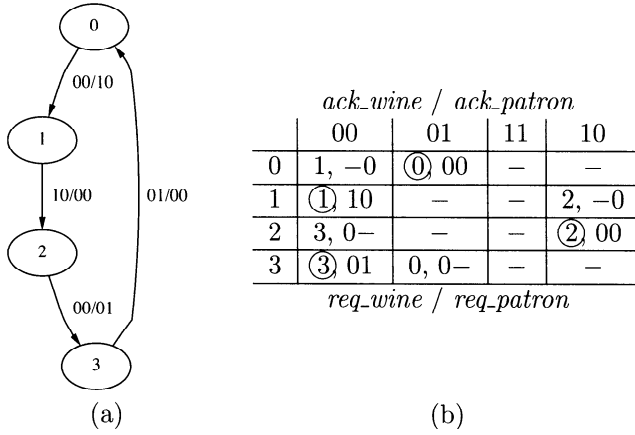


Fig. 1.11 (a) AFSM and (b) Huffman flow table for active/active shop (input/output vector is  $\langle ack\_wine, ack\_patron \rangle / \langle req\_wine, req\_patron \rangle$ ).

 


Fig. 1.12 Reduced (a) AFSM and (b) Huffman flow table for active/active shop.

reduce the number of states in the state machine. This process is called *state minimization*. The new AFSM and flow table are shown in Figure 1.12.

Next, we must choose a *state assignment* for our two states. This is a unique binary value for each state. Now, care must be taken when doing this for an asynchronous design, but for this simple design only a single bit is needed. Therefore, encoding state 0 with '0' and state 1 with '1' suffices here.

At this point, it is a simple matter to derive the circuit by creating and solving three *Karnaugh maps* (K-maps). There is one for each output and one for the state signal as shown in Figure 1.13. The circuit implementation is shown in Figure 1.14.

Let's compare this circuit with the one shown in Figure 1.10. The logic for *req\_wine* and *req\_patron* is identical. The logic for *x* is actually pretty similar to that of the preceding circuit except that Huffman sticks with simple AND and OR gates. "Muller's C-element is cute, but it is really hard to find in any of the local electronics shops" says Dr. Huffman. Also, all of Huffman's delay elements have an upper bound, *U*. Huffman assumes a *bounded gate and wire delay model*. Huffman's circuit is also not closed. That is, he does

<i>ack_wine/ack_patron</i>					<i>ack_wine/ack_patron</i>					<i>ack_wine/ack_patron</i>				
<i>x</i>	00	01	11	10	<i>x</i>	00	01	11	10	<i>x</i>	00	01	11	10
0	1	0	—	—	0	0	0	—	0	0	0	—	—	1
1	0	0	—	0	1	1	—	—	0	1	1	0	—	1
<i>req_wine</i>					<i>req_patron</i>					<i>x</i>				

Fig. 1.13 K-maps for active/active shop.

 


Fig. 1.14 Huffman's circuit for active/active shop.


not explicitly show the relationships between the outputs and inputs, which is not necessary in his method. Huffman also splits the feedback into an output signal,  $X$ , and an input signal,  $x$ .

These are the obvious differences. There are also some not so obvious ones: namely, Huffman's assumptions on how this circuit will be operated. First, Huffman assumes that the circuit is operated in what is called *single-input-change fundamental mode*. What this means is that the environment will apply only a single input change at a time; it will not apply another until the circuit has stabilized. In other words, the operation of the circuit is as follows: An input changes, outputs and next-state signals change, the next state is fed back to become the current state, and then a new input can arrive. To maintain this order, it may not only be necessary to slow down the environment, but it may also be necessary to delay the state signal change from being fed back too soon by adding a delay between  $X$  and  $x$ .

Consider again the bad trace. Again, the following sequence can happen:

$$\begin{aligned} & req\_wine+, ack\_wine+, X+, x+, req\_wine-, \\ & ack\_wine-, req\_patron+, ack\_patron+. \end{aligned}$$

At this point,  $u2$  and  $u6$  are again enabled to go to '0', and let's assume that the delay of  $u2-$  is faster than that of  $u6-$ . After  $u2$  becomes '0',  $X$  can go to '0' before  $u6$  goes to '0'. However, in this case, we have added sufficient delay in the feedback path such that we do not allow  $x$  to change to '0' until we have ensured that the circuit has stabilized. In other words, as long as the delay in the feedback path is greater than  $U$ , the glitch does not occur.

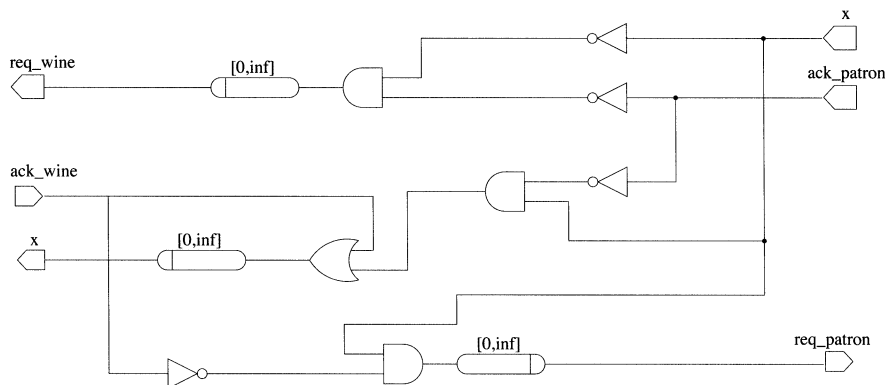

*Fig. 1.15* Muller's circuit for active/active shop.

## 1.7 MULLER CIRCUITS

“What kind of crazy ideas have you been putting in this poor man’s head?”,

"Well, if it isn't Dr. Muller. You're late as usual," announced Dr. Huffman.

“You know me, I don’t believe in bounding time. Let me take a look at what you got there,” said Dr. Muller. He stared at the napkin and made some marks on it. “Now, that’s much better. Take a look at this” (see Figure 1.15).

Muller's circuit looks similar to Huffman's, but there are some important differences in Muller's model. First, notice that he removed the delay elements from the wires, leaving only a single delay element on each output and next-state signal. He also changed the upper bound of this delay element to infinity. Finally, he changed the signal  $X$  to  $x$ . In his circuit, Muller has not put any restrictions on the order that inputs, outputs, and state signals change except they must behave according to the protocol. This model is called an *unbounded gate delay* model. Note that in this model, Muller assumes that wire delays are negligible. This means that whenever a signal changes value, all gates it is connected to will see that change immediately. For example, *ack\_wine* and *ack\_patron* each fork to two other gates while  $x$  forks to three. These forks are called *isochronic forks*, meaning that they have no delay. This delay model is called *speed-independent*. A similar model where only certain forks are isochronic is called *quasi-delay insensitive*.

Consider again the bad trace. The following sequence can still happen: *req\_wine+*, *ack\_wine+*, *x+*, *req\_wine-*, *ack\_wine-*, *req\_patron+*, *ack\_patron+*. At this point, the gates for *req\_wine* and *x* see the change in *ack\_patron* at the same time, due to the isochronic fork. Therefore, when *x* goes to '0', the effect of *ack\_patron* being '1' is already felt by *req\_wine*, so it does not glitch to '1'. The circuit is hazard-free under Muller's model as well, and he did not need to determine any sort of delay for the state variable feedback path.

"Those isochronic forks can be tricky to design," insisted Dr. Huffman.



This is true. Both models require some special design. By the way, not all the forks actually need to be isochronic. In particular, you can put different delays on each of the branches of the wire fork for  $x$  and the circuit still operates correctly.

## 1.8 TIMED CIRCUITS

The engineer returned from the bar where he had been talking to the wine patron and the head of production from the winery. He learned a few interesting things which can be used to optimize the circuit. First, he learned that with the winery's new wine production machine, they are always well ahead of schedule. In fact, since they are only one block away from the wine shop, they have guaranteed delivery within 2 to 3 minutes after being called. The patron lives about five blocks away and it takes him at least 5 minutes to get to the shop after being called. If he is busy sleeping one off, it may take him even longer. Finally, the circuit delays will all be very small, certainly less than 1 minute. Using this delay information and doing a bit of reshuffling, he came up with this description of the circuit and its environment:

```
Shop_AA_timed:process
begin
  assign(req_wine,'1',0,1);  -- call winery
  assign(req_patron,'1',0,1); -- call patron
  -- wine arrives and patron arrives
  guard_and(ack_wine,'1',ack_patron,'1');
  assign(req_wine,'0',0,1);
  assign(req_patron,'0',0,1);
  -- wait for ack_wine and ack_patron to reset
  guard_and(ack_wine,'0',ack_patron,'0');
end process;
winery:process
begin
  guard(req_wine,'1');      -- wine requested
  assign(ack_wine,'1',2,3); -- deliver wine
  guard(req_wine,'0');
  assign(ack_wine,'0',2,3);
end process;
patron:process
begin
  guard(req_patron,'1');      -- shop called
  assign(ack_patron,'1',5,inf); -- buy wine
  guard(req_patron,'0');
  assign(ack_patron,'0',5,7);
end process;
```

The assignment function now takes two additional parameters, which are the lower and upper bounds on the delay the assignment takes to complete.

 


Fig. 1.16 TEL structure for active/active shop.

The **guard\_and** function requires multiple signals to attain a given value before the circuit can progress. Notice that in this protocol, the patron is called after the wine is requested but before the wine arrives. This improves the performance of the system by allowing more concurrency. As we will see, timing assures that the patron does not arrive too early.

The TEL structure for this specification is shown in Figure 1.16. Assume that all signals are initially low. In the TEL structure, there are timing annotations on each arc. For example, *req\_wine* must go to '1' within 0 to 1 minute from the initial state. Once *req\_wine* has gone to '1', *ack\_wine* can go to '1' since its level expression is now true. However, it must wait at least 2 minutes and will change within 3 minutes. The signal *req\_patron* is also enabled to change and will do so within 0 to 1 minute. Therefore, we know that *req\_patron* will change first. After *req\_patron* has gone to '1', *ack\_patron* is now enabled to change to '1', but it must wait at least 5 minutes. Therefore, we know that *ack\_wine* changes next. In other words, we know that the wine will arrive before the patron arrives—a very important property of the system.

From this TEL structure, we derive the state graph in Figure 1.17. In the initial state, all signals are 0, but *req\_wine* is labeled with an R to indicate that it is enabled to rise. Once *req\_wine* rises, we move to a new state where *req\_patron* and *ack\_wine* are both enabled to rise. However, as mentioned before, the only possible next-state transition is on *req\_patron* rising.

To get a circuit, a K-map is created for each output with columns for each input combination and rows for each output combination. A 1 is placed in each entry, corresponding to a state where the output is either R or 1, a 0 in each entry where the output is F or 0, and a – in the remaining entries. From the maps in Figure 1.18, the simple circuit in Figure 1.19 is derived. Note that the signal *ack\_wine* is actually no longer needed.

 


Fig. 1.17 State graph for active/active shop (with state vector  $\langle \text{ackwine}, \text{ackpatron}, \text{reqwine}, \text{reqpatron} \rangle$ ).

 


Fig. 1.18 K-maps for active/active shop.

 


Fig. 1.19 Timed circuit for active/active shop.

## 1.9 VERIFICATION

The timed circuit made some pretty aggressive assumptions. How does one know if the circuit operates correctly? The first thing to do is to simulate the circuit for some example situations and check that all parties end up happy. This process is *validation*. However, to be really sure, one must exhaustively check all possible situations. This process is *formal verification*. First, one can check that the circuit always does what it is specified to do. In this case, we say that a circuit *conforms* to its specification. In other words, the circuit should follow the protocol. However, this may not be sufficient for the shopkeeper to rest easy on the Maui beaches. For example, in the modified protocol, if the timing assumptions are violated, it is possible for the patron to arrive before the wine. Knowing how irate he gets when this happens, this is clearly not acceptable. Therefore, one should enumerate the properties that the circuit should have and check that the protocol with the timing assumptions satisfies these properties. This process is called *model checking*. Two such properties might be these:

1. The wine arrives before the patron.
2. When the wine is requested, it eventually arrives.

Both of these properties hold for all states in Figure 1.17.

## 1.10 APPLICATIONS

With all these design alternatives, how does one know which one to choose? You may want to choose the fastest. In a synchronous design, you simply determine the worst-case delay and set your clock cycle to match. Recall that in synchronous wine shopping that the patron received one bottle of wine each hour independent of the speed of production. In an asynchronous circuit, however, it is not that simple to determine performance since you must consider average performance. Let us assume that the delays are those used in the timed circuit and are uniformly distributed over their range, except that the patron's delay in buying the wine actually ranges uniformly between 5 and 10 minutes (it may be more, but that is pretty unlikely). If this is the case, we find that the protocol used by Huffman and Muller has a cycle time of 21.5 minutes on average, while our original one (*ShopAAreshuffled*) had a cycle time of 20.6 minutes. These means that for these asynchronous designs the patron will receive on average 3 bottles of wine per hour, a substantial improvement over synchronous shopping. The timed circuit's cycle time is only 15.8 minutes. This means that on average the patron will get even one more bottle of wine every hour using the timed circuit!

## 1.11 LET'S GET STARTED

"Anyway, this is enough talk about work for now. What do you say that we order some dinner?" said the engineer.

"This is just getting interesting. I would like to learn more," said the shopkeeper.

"Why don't you attend our seminar at the local university?" replied the engineer.

Did the shopkeeper attend the seminar? Did he and his wife ever get that trip to Maui? Did they ever get their dinner? To learn more, you must read the next chapter.

## 1.12 SOURCES

Detailed references on the material in this chapter are given at the end of subsequent chapters when these topics are discussed. The idea of modeling communicating processes through send and receive actions on channels originated with Hoare's *communicating sequential processes* (CSP)[166, 167] and was adapted to the specification of asynchronous circuits by Martin [254]. The Huffman flow table is described in [170] (republished later in [172]). Petri nets were introduced in [312], and they were first adapted to the specification of asynchronous circuits by Seitz [343]. TEL structures were introduced by Belluomini and Myers [34].

In [253], Martin proved that when the gate library is restricted to single-output gates, the class of circuits that can be built using a purely delay-insensitive (DI) model is severely limited. Namely, these circuits can only utilize inverters and *Muller C-elements*. This result and the examples contained in this paper inspired much of the discussion in this chapter. Similar results appeared in [54]. This paper also shows that set-reset latches, C-elements, and toggles cannot be implemented delay insensitively using basic gates (i.e., combinational gates). Leung and Li extend these results and show that when a circuit is not closed (i.e., some input comes from an outside environment and not another gate in the circuit), other gates, such as AND and OR gates, can be used in a limited way [230]. They also show that arbitrary DI behaviors can be implemented using a set of circuit elements that includes an inverter, fork, C-element, toggle, merge, and asynchronous demultiplexer.

Techniques using the fundamental-mode assumption originated with Huffman [170, 172]. The speed-independent model was first proposed by Muller and Bartky [279], and it was used in the design of the ILLIAC and ILLIAC II [46]. In [282], Myers and Meng introduced the first synthesis method which utilized a timed circuit model to optimize the implementation. Earlier, however, most practical asynchronous designs certainly utilized timing assumptions in an ad hoc fashion to improve the implementation.

## Problems

- 1.1** Describe in words the behavior of the channel-level process given below.

```
Shop:process
begin
  receive(WineryShop,bottle1);
  receive(WineryShop,bottle2);
  send(ShopPatron,bottle2);
  send(ShopPatron,bottle1);
end process;
```

- 1.2** In this problem we design a Huffman circuit for the shop when the winery is passive while the patron is active.

**1.2.1.** Write a process for a four-phase active/passive shop.

- 1.2.2.** A reshuffled version of an active/passive shop is shown below. Give an AFSM and Huffman flow table that describe its behavior.

```
Shop_AP_reshuffled:process
begin
  guard(req_patron,'1'); -- patron calls
  assign(req_wine,'1');  -- call winery
  guard(ack_wine,'1');   -- wine arrives
  assign(req_wine,'0');  -- reset req_wine
  guard(ack_wine,'0');   -- ack_wine resets
  assign(ack_patron,'1'); -- sells wine
  guard(req_patron,'0'); -- req_patron resets
  assign(ack_patron,'0'); -- reset ack_patron
end process;
```

**1.2.3.** Combine compatible rows and make a state assignment.

**1.2.4.** Use K-maps to find a Huffman circuit implementation.

- 1.3** In this problem we design a Muller circuit for the shop when the winery is passive while the patron is active.

**1.3.1.** Draw a TEL structure for the reshuffled active/passive shop below.

```
Shop_AP_reshuffled:process
begin
  assign(req_wine,'1');  -- call winery
  guard(ack_wine,'1');   -- wine arrives
  guard(req_patron,'1'); -- patron calls
  assign(ack_patron,'1'); -- sells wine
  assign(req_wine,'0');  -- reset req_wine
  guard(ack_wine,'0');   -- ack_wine resets
  guard(req_patron,'0'); -- req_patron resets
  assign(ack_patron,'0'); -- reset ack_patron
end process;
```

**1.3.2.** Find the state graph from the TEL structure.

**1.3.3.** Use K-maps to derive a Muller circuit implementation.